


Chapter 2

Textbook questions

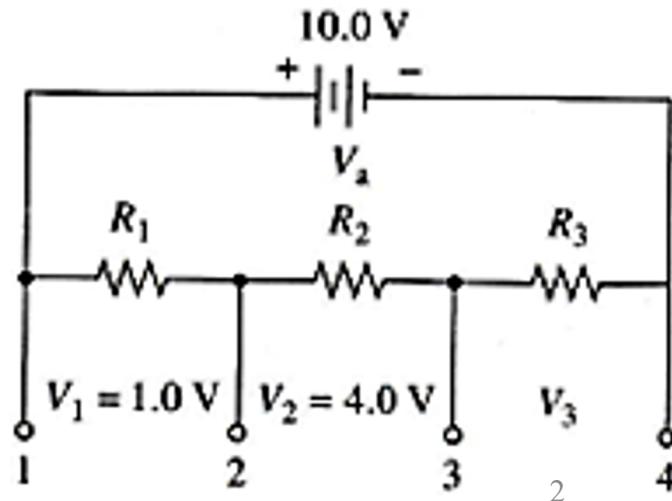Question 2-1

For assembling the voltage divider shown below, two of each of the following resistors are available: 250Ω , 500Ω , $1.0k\Omega$.

- Describe a suitable combination of the resistors that would give the indicated voltages.
- What would be the IR drop across R_3 ? Note: R_3 could be more than one resistor
- What current would be drawn from the source?
- What power is dissipated by the circuit?



250Ω, 500Ω, 1.0kΩ

Question 2-1 a)

Voltage divider equation:

$$\frac{V_1}{V} = \frac{R_1}{R_1 + R_2 + R_3}$$

$$V_1 = 1.0V \quad \frac{1}{10} = \frac{R_1}{R_1 + R_2 + R_3}$$


$$V_2 = 4.0V \quad \frac{4}{10} = \frac{R_2}{R_1 + R_2 + R_3}$$

$$V_3 = ? \quad V_3 = 10.0V - 1.0V - 4.0V = 5.0V$$

$$\frac{5.0}{10} = \frac{R_3}{R_1 + R_2 + R_3}$$

$$R_1/R_2 = 1.0/4.0$$

$$R_2/R_3 = 4.0/5.0$$

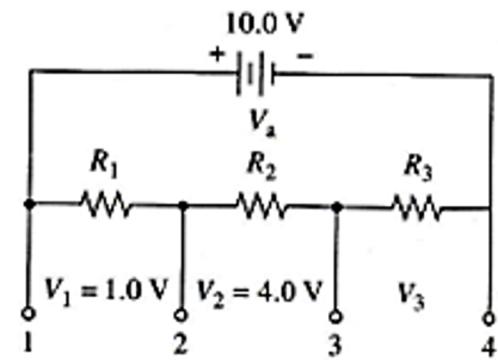


$$\text{Let } R_1 = 250\Omega$$

$$R_2 = 250 \times 4 = 1000\Omega = 1.0k\Omega$$

$$R_3 = 1000 \times (5.0/4.0) = 1250\Omega = 1.25k\Omega$$

Therefore 250Ω and 1.0kΩ resistor are used

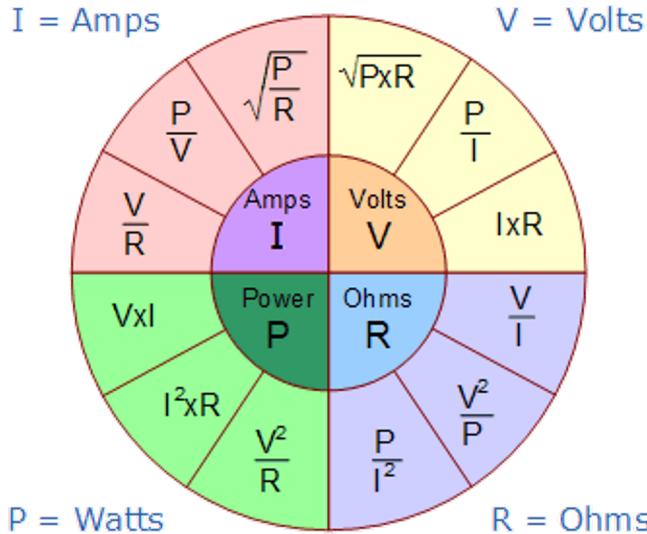

Question 2-1 b), c), d)


(b) $V_3 = IR_3 = 10.0 \text{ V} - 1.0 \text{ V} - 4.0 \text{ V} = 5.0 \text{ V}$

(c) $I = V/(R_1 + R_2 + R_3) = 10.0 \text{ V}/(250 \Omega + 1000 \Omega + 1250 \Omega) = 0.004 \text{ A (4.0 mA)}$

(d) $P = IV = 0.004 \text{ A} \times 10.0 \text{ V} = 0.04 \text{ W}$ (Equation 2-2)

Question 2-2



- What is voltage V_2 ?
- What would be the power loss in resistor R_2 ?
- What fraction of the total power lost by the circuit would be dissipated in resistor R_2 ?

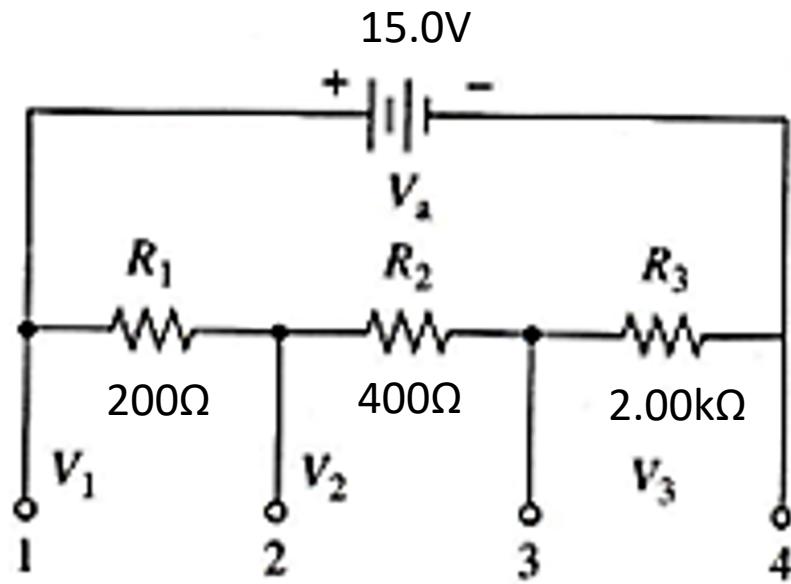

Question 2-2

- (a) From Equation 2-10, $V_2 = 15 \times 400 / (200 + 400 + 2000) = 2.31 \text{ V}$
- (b) $P = V_2^2 / R_2 = (2.31)^2 / 400 = 0.013 \text{ W}$
- (c) Total $P = V^2 / R_s = (15)^2 / 2600 = 0.087 \text{ W}$


Percentage loss in $R_2 = (0.013 / 0.087) \times 100 = 15\%$

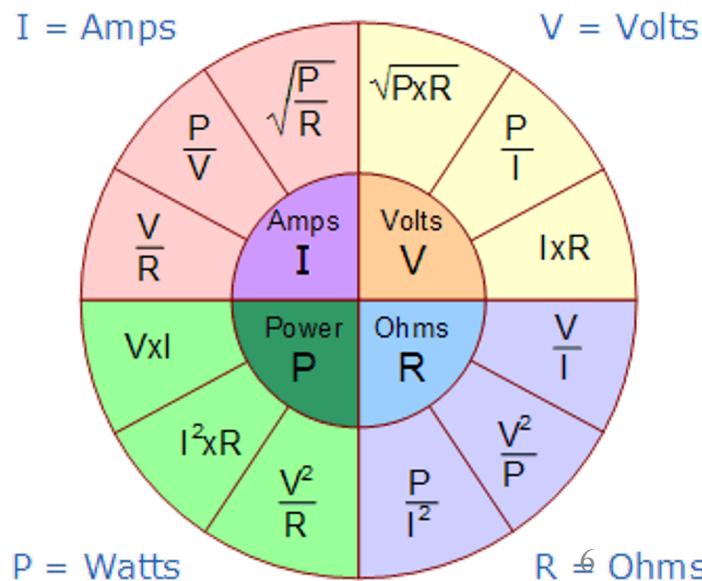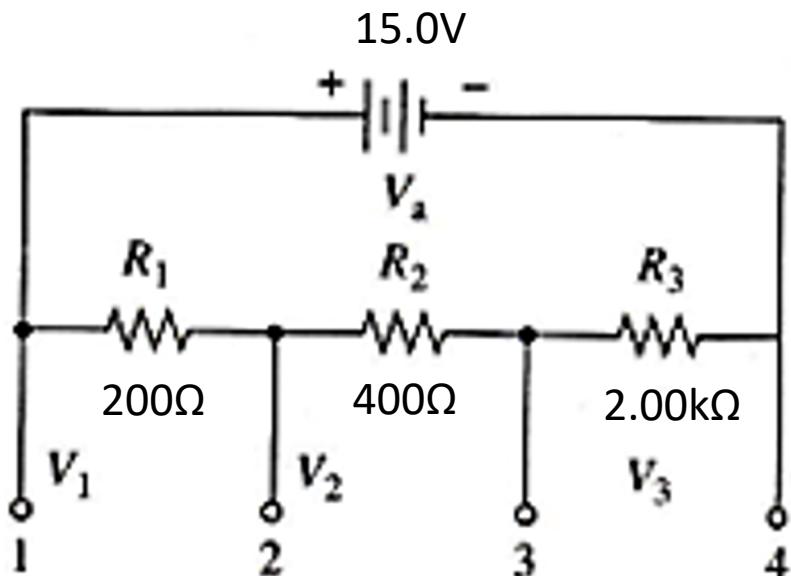

Question 2-3

For a circuit similar to the one shown in Problem 2-1, $R_1 = 1.00 \text{ k}\Omega$, $R_2 = 2.00 \text{ k}\Omega$, $R_3 = 4.00 \text{ k}\Omega$, and $V_a = 24.0 \text{ V}$. A voltmeter was placed across contacts 2 and 4. Calculate the relative error in the voltage reading if the internal resistance of the voltmeter was:

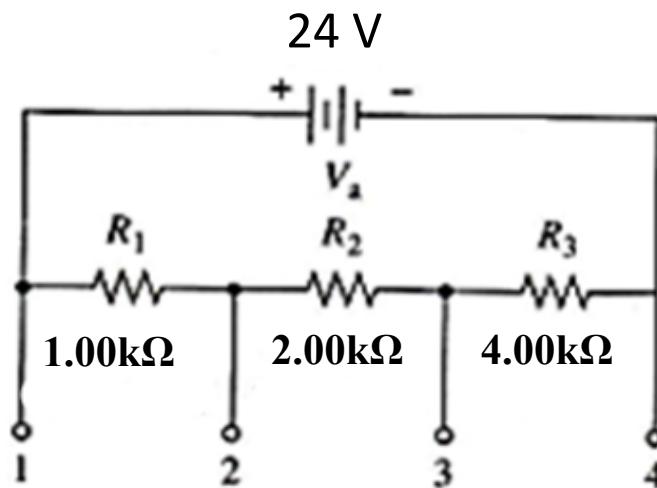- a) 4000Ω
- b) $80.0 \text{ k}\Omega$
- c) $1.00 \text{ M}\Omega$



$$\text{Relative error} = \frac{V_{\text{measure}} - V_{\text{Theo}}}{V_{\text{Theo}}} \times 100\%$$

Question 2-3


$$V_{2,4} = 24.0 \times [(2.0 + 4.0) \times 10^3] / [(1.0 + 2.0 + 4.0) \times 10^3] = 20.6 \text{ V}$$

With the meter in parallel across contacts 2 and 4,

$$\frac{1}{R_{2,4}} = \frac{1}{(2.0 + 4.0) \text{ k}\Omega} + \frac{1}{R_M} = \frac{R_M + 6.0 \text{ k}\Omega}{R_M \times 6.0 \text{ k}\Omega}$$

$$R_{2,4} = (R_M \times 6.0 \text{ k}\Omega) / (R_M + 6.0 \text{ k}\Omega)$$
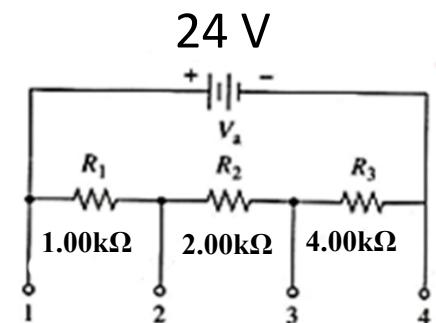
$$(a) R_{2,4} = (4.0 \text{ k}\Omega \times 6.0 \text{ k}\Omega) / (4.0 \text{ k}\Omega + 6.0 \text{ k}\Omega) = 2.40 \text{ k}\Omega$$



$$V_M = (24.0 \text{ V} \times 2.40 \text{ k}\Omega) / (1.00 \text{ k}\Omega + 2.40 \text{ k}\Omega) = 16.9 \text{ V}$$

$$\text{rel error} = \frac{16.9 \text{ V} - 20.6 \text{ V}}{20.6 \text{ V}} \times 100\% = -18\%$$

- (b) -1.2% (c) -0.2%

Question 2-4

A voltmeter was used to measure the voltage of a cell with an internal resistance of $1.00\text{k}\Omega$. What must the internal resistance of the meter be if the relative error in the measurement is to be less than

- a) -1.0%
- b) -0.10%

$$E_r = \frac{-R_s}{R_M + R_s} \times 100\%$$

Question 2-4

$$(a) -1.0\% = -\frac{1000 \Omega}{(R_M + 1000 \Omega)} \times 100\%$$

$$R_M = (1000 \times 100 - 1000) \Omega = 99000 \Omega \text{ or } 99 \text{ k}\Omega$$

$$(b) -0.1\% = -\frac{1000 \Omega}{(R_M + 1000 \Omega)} \times 100\%$$

$$R_M = 999 \text{ k}\Omega$$

Chapter 3

Textbook questions

Question 3-1

An operational amplifier has output voltage limits of +13V and -14V when used with a ± 15 V power supply. If the amplifier is used as comparator, by what amount does v_+ have to exceed v_- and v_- have to exceed v_+ for the amplifier to be at limit if the open-loop gain A is


- a) 100000
- b) 600000
- c) 2.6×10^6

$$v_o = A v_s$$

V_s = input difference voltage

$$v_s = (v_+ - v_-)$$

$$v_o = A v_s = A(v_+ - v_-)$$

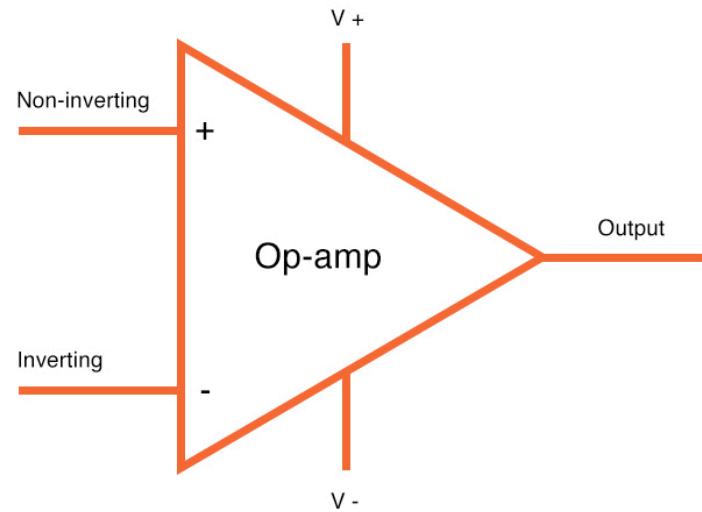

Question 3-1

$v_o = Av_s = A(v_+ - v_-)$ For + limit, $+13 \text{ V} = A(v_+ - v_-)$. For - limit, $-14 \text{ V} = A(v_+ - v_-)$.

- (a) If $A = 100,000$, for + limit, $(v_+ - v_-) = 13 \text{ V}/100,000 = 130 \mu\text{V}$. So v_+ must exceed v_- by $130 \mu\text{V}$ for + limit to be reached.


For - limit, $(v_+ - v_-) = -14 \text{ V}/100,000 = -140 \mu\text{V}$, v_- must exceed v_+ by $140 \mu\text{V}$.

- (b) For + limit $(v_+ - v_-) = 13 \text{ V}/600,000 = 21.7 \mu\text{V}$. For - limit $(v_+ - v_-) = -14 \text{ V}/600,000 = -23.3 \mu\text{V}$.

- (c) + limit, $(v_+ - v_-) = 13 \text{ V}/2.6 \times 10^6 = 5.0 \mu\text{V}$; - limit, $(v_+ - v_-) = -14 \text{ V}/2.6 \times 10^6 = -5.4 \mu\text{V}$

Question 3-7

In the following circuit, R is a variable resistor. Derive an equation that describes v_o as a function of v_i and the position x of the movable contact of the voltage divider. Perform the derivation such that x is zero if there is zero resistance in the feedback loop.

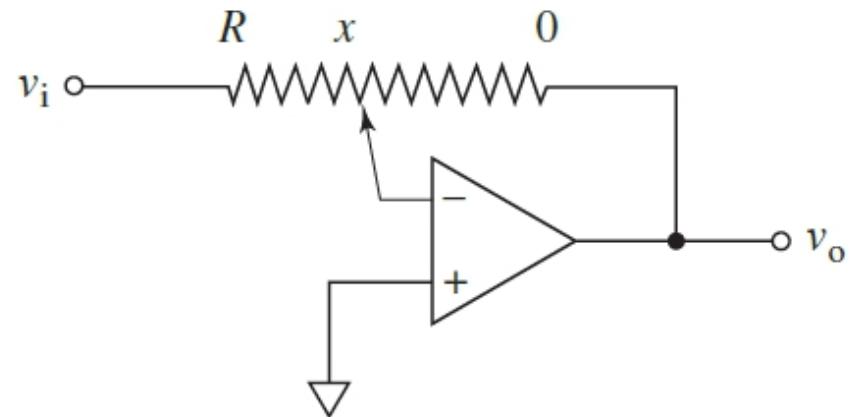

Question 3-7

$$v_o = -ix$$

$$v_i = i(R - x)$$

$$\frac{v_o}{v_i} = \frac{-ix}{i(R-x)} = -\frac{x}{R-x}$$

$$v_o = -\left(\frac{x}{R-x}\right)v_i$$

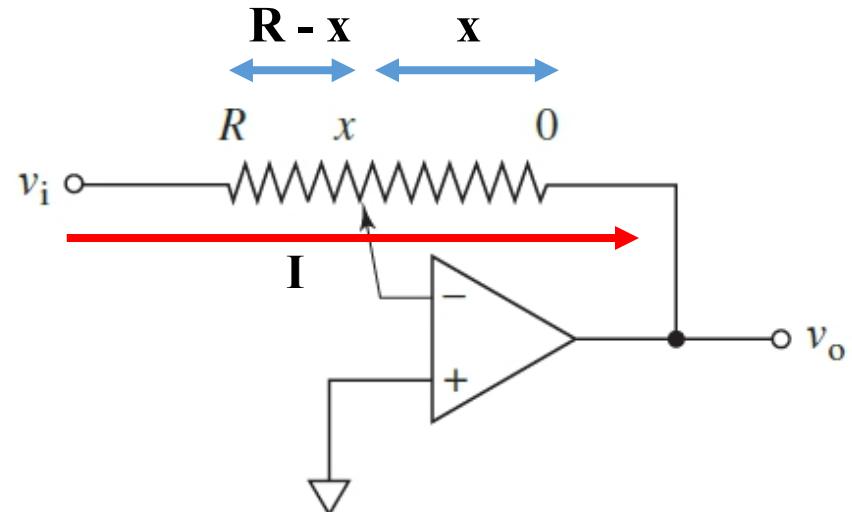


Figure 3-7

