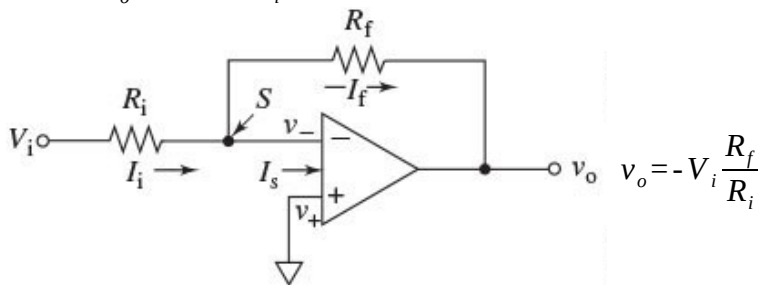


Name: _____

ID: _____

Analytical Chemistry II – Quiz (16th March, 2021)

1) How does v_o relate to V_i in this circuit? Write down the formula.



2) List four main sources of instrumental noise in analytical measurements.

thermal noise

shot noise

flicker (1/f) noise

environmental noise